

- [home](#)
- [electronics](#)
- [howto](#)
- [tools](#)
- [knowledge](#)

Dual H-bridge Motor Driver - L293D IC

Parts required


Parts	Details	Quantity
 <div> L293D IC L293D Motor Driver IC </div>	Motor Driver IC	1
 <div> 16 Pin Socket 16 Pin Socket Perforated board </div>	<div>8x2 DIP Socket</div> <div>With 20x12 or more holes</div>	<div>1</div> <div>1</div>



[Perforated board](#)
[Connecting wires](#)




[Wire](#)

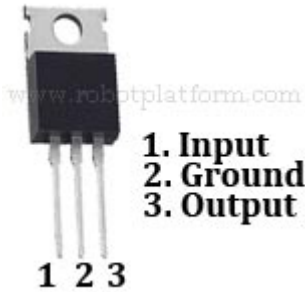

[7805](#)
[7805](#)

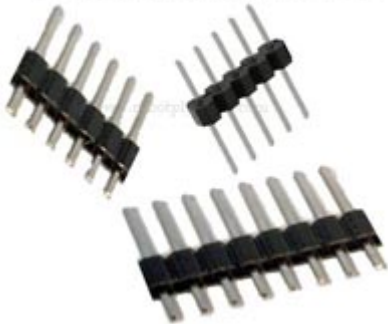[Male breakaway headers](#)
Breakaway Male Headers



[Male Breakaway Headers](#)
[Solder](#)



[Solder Lead](#)

Any color of your choice

10-12 small pieces

Linear Voltage Regulator

1

40 pin single row headers

1

Lead / Lead free

50-100 gms

Solder Iron

Preferably temperature controlled


1




Solder Iron

Building the circuit - Part I

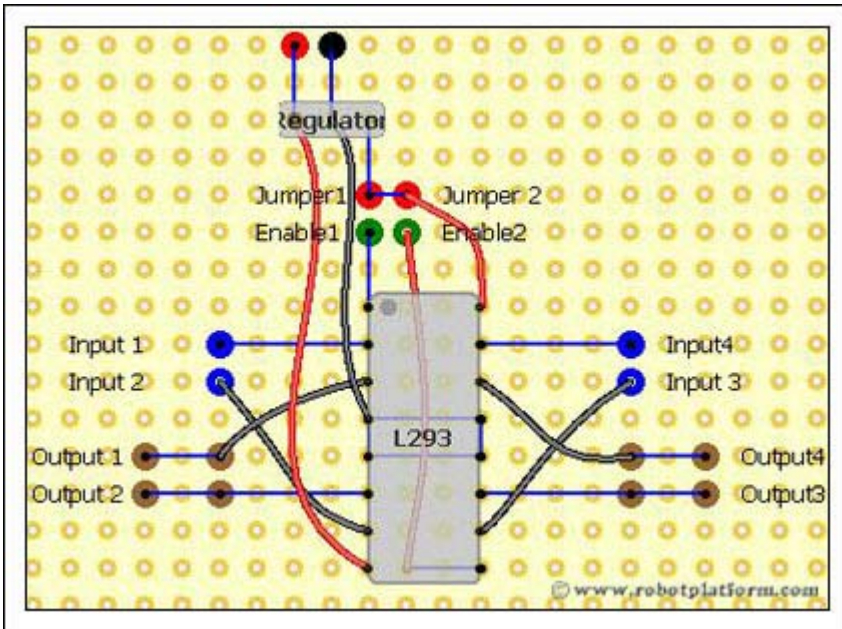Before building the circuit, I prefer using [DIY Layout Editor](#) to replicate the circuit. DIY Layout Editor is a free PCB design tool which I would highly recommend if you are someone who works like me :)



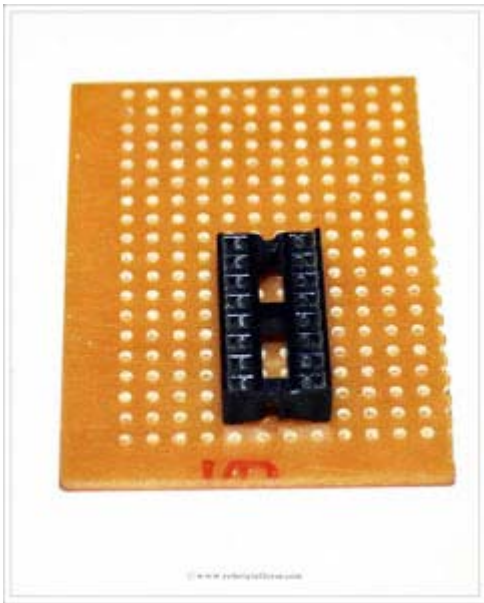Let's begin building the circuit. First, add 16 pin socket to the board as shown in the image. As usual, click on any image for an enlarged view with higher resolution. If the step requires soldering, then the soldered part is highlighted to help you with soldering.



Solder first and 16th pin of the socket to copper side of the board.




Add two 2-pin headers (two 2 pin headers) to the left of socket. Make sure there is at least a gap of two holes between socket and header.




Solder horizontal pins together.

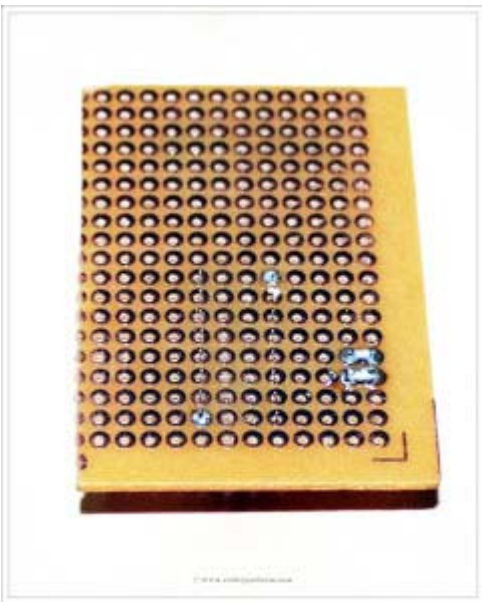
The vertical two pins will be later used to connect the first motor. The other two pins are there in case we need to use this output for some other reason. If you do not need this, you can use a single 2-pin header and plug it vertically and individually solder the two pins to the board.



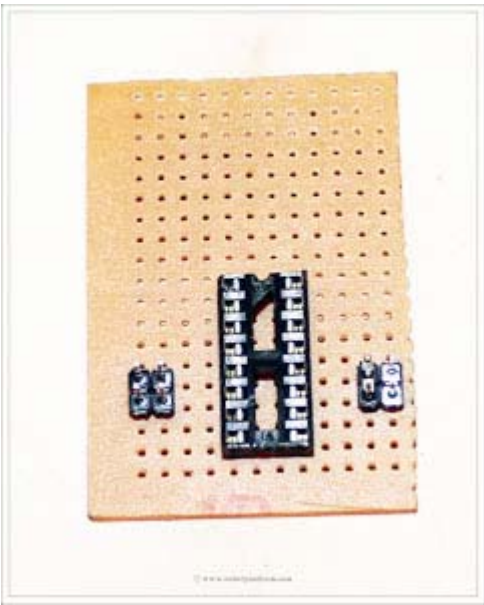
Add two more 2-pin headers to the right side of the socket with a minimum gap of two holes between socket and header. The gap makes it easier to plug other female headers once the board is completed.



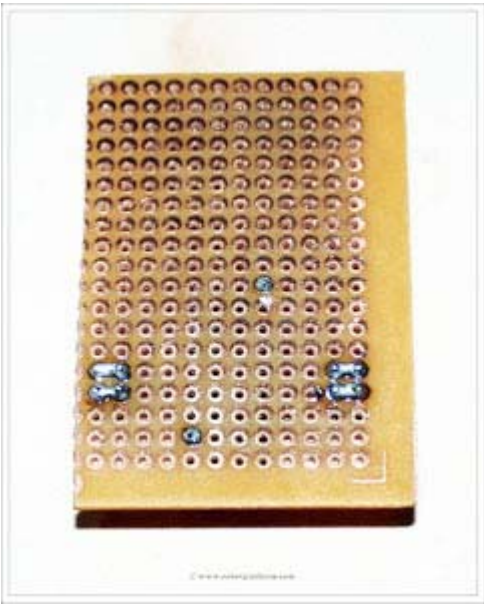
Solder these two headers similar to the left headers



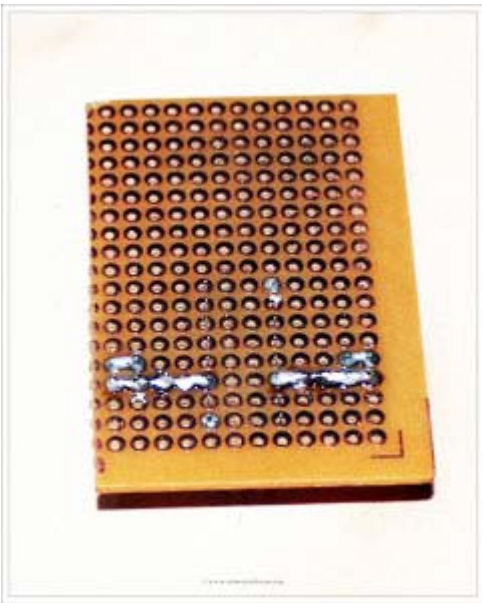Now solder the bottom pins of two headers on either side to Pin6 and Pin11 of the IC, as shown in the image.



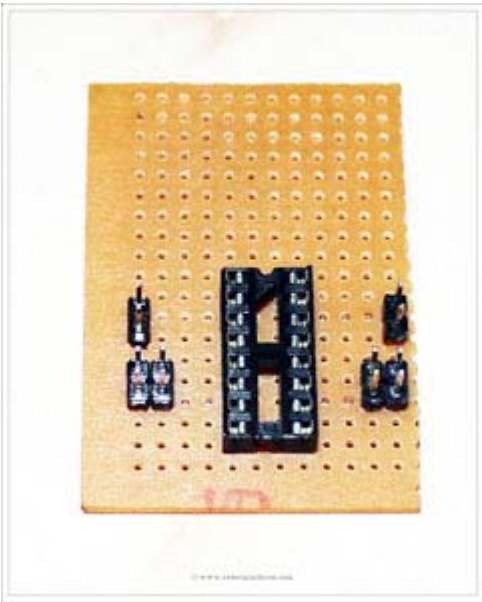
Add two more 2-pin headers to either side of the board. These two headers are input pins which are later connected to microcontroller.



Solder each pin of the header to the board, but take care not to solder them together. As shown in the image, solder the top two header pins on either side to Pin2 and Pin15 respectively.




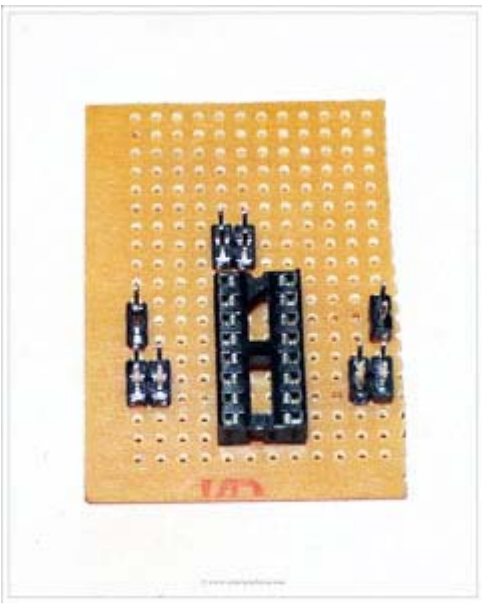We need two more 2-pin headers, one header for **enable pins** and other for +5V. Push the two 2-pin headers as pictured below. Let the first two vertical pins be in the same line as the socket pins.




Observe carefully how the soldering happens from here on if you are not sure what is happening. I can assure that you would have a complete working circuit if you follow the tutorial exactly.

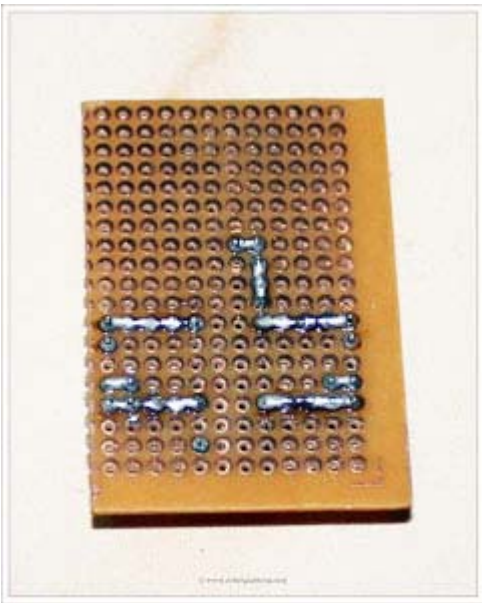
The top two header pins are soldered together. One of the pin in bottom header is soldered to Pin1 of the socket. Click on the image to understand what I mean.



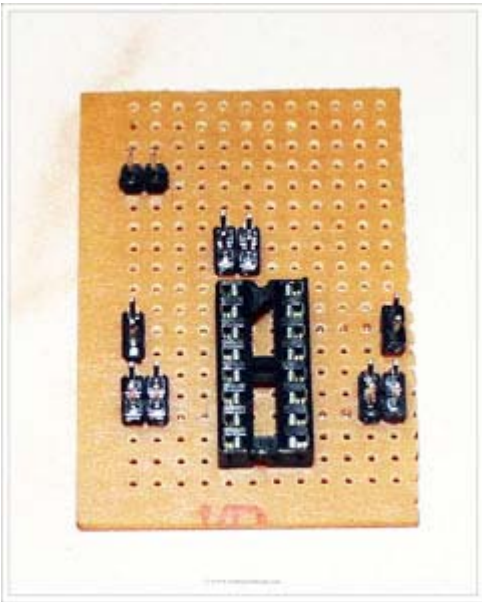We will add two more pins for powering the circuit (we will call these two pins as **Power pins** to make soldering easier).




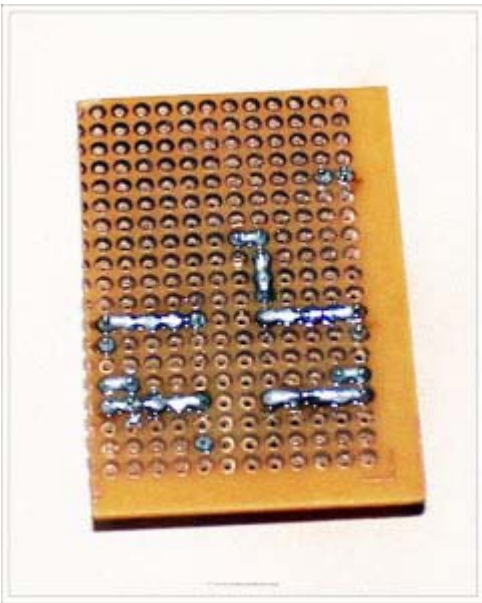Solder each pin of the header to the board, but do not short them.




Add a 7805 voltage regulator such that the center pin is in line with power pins. I have bent the regulator to make it look compact (or I just like to keep it like that). If you do not want to bend it, keep it upright.

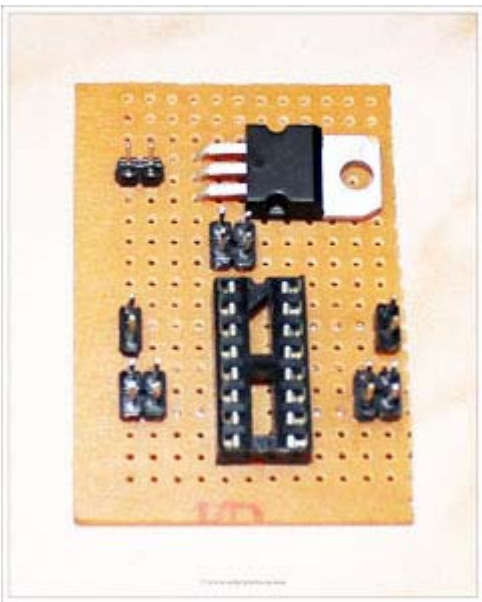The top lead of regulator is input (Vin), middle lead is ground (Gnd) and the bottom lead is output (Vout) which gives a regulated +5volts.



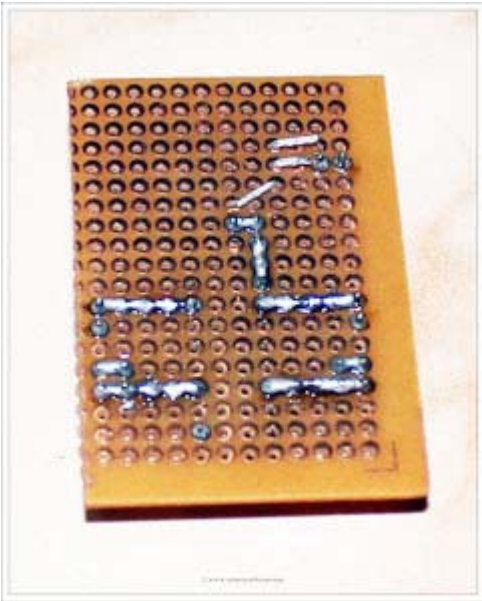Bend the regulator leads as shown. The middle pin almost touches one of the power pins. If the regulator lead (the middle one) is too long such that it touches both the power pins, cut it short. Vin should also be bent in the same fashion. Vout is bent such that it touches the headers above enable pins.



Tutorial index:

1. [Motor Driver and H-bridge basics](#)
2. [Parts required and Building the circuit - Part I](#)
3. [Building the circuit - Part II](#)

«[Previous](#) - § - [Next](#)»

Do you have anything to say?

Visit the [Forum](#) to discuss, learn and share anything related to robotics and electronics !!



Featured Videos

Servo and AVR microcontroller - Atmega8



Advertisements

Recent Articles

[Atmega8 Development Board](#)

A great step-by-step tutorial on building your own Atmel AVR based Atmega8 development board. The board is ideal for beginners with detailed explanation and pictures [More...](#)

[L293D Motor Driver](#)

For robots to do work, you need to know how to control a motor. L293D is a cleverly packed IC which can control two DC motors in both directions: forwards and reverse. Here is a detailed explanation of building a board based on L293D IC [More...](#)

[Hobby Servo Tutorial](#)

Servo Motor is a device which uses error-sensing feedback signals to determine and control the position of a motor shaft. The term "servomechanism" closely relates to servo motors.. [More...](#)

[Blinking LED Tutorial](#)

This is similar to what we achieve in any "Hello World" program. However, it is not just limited to blinking LED but scratches the surface of AVR-GCC programming... [More...](#)

Kindly Donate

If this site has helped you, then kindly consider a Donation to say "Thank You!!". Donation might help us keep all this information available for free and also pay for the resources.

If that is difficult, then a simple "Hi" in the [forum](#) would still do good :)

Five US Dollars \$5.00 USD ▼

Pay Now



[HOME](#) | [ELECTRONICS](#) | [HOWTO](#) | [KNOWLDGE](#) | [TOOLS](#) | [FORUM](#)

[Contact Us](#) | [Disclaimer & Privacy](#) | [Sitemap](#)

© Copyright 2010 - 2022 [ROBOT PLATFORM](#) All Rights Reserved

